



KUZEY KIBRIS  
KAMPÜSÜ

**ODTÜ  
METU**

NORTHERN CYPRUS  
CAMPUS


## **Lab 7 Report**

**Name:** Muhammad Somaan

**ID:** 2528404

# FSM)

State diagram:

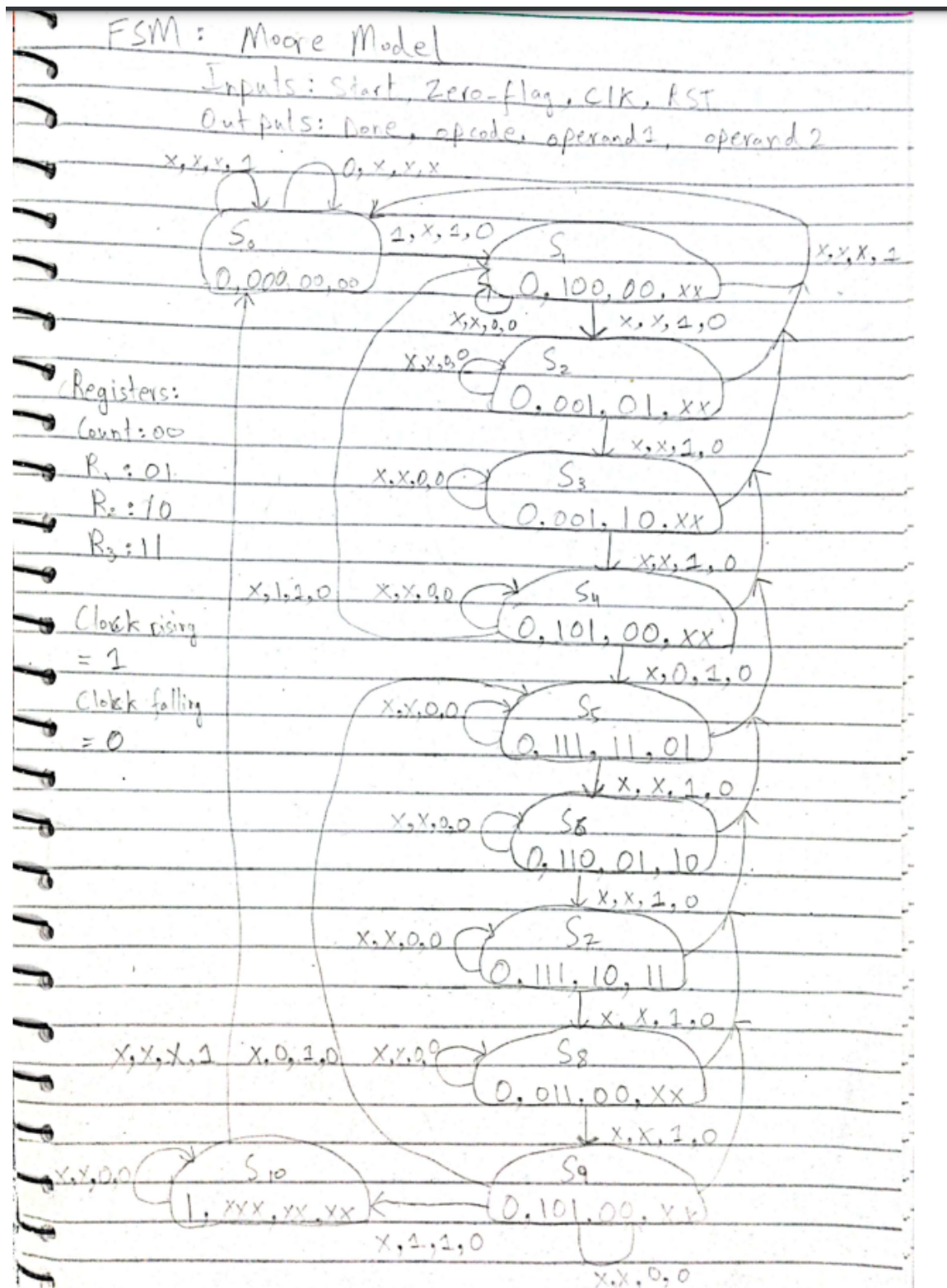

## State Table:

States	Inputs				Outputs			
	0,x,x,1	1,1,1,0	1,0,1,0	x,x,1,1	Done	opcode	op1	op2
S <sub>0</sub>	S <sub>0</sub>	S <sub>1</sub>	S <sub>1</sub>	S <sub>0</sub>	0	000	00	00
S <sub>1</sub>	S <sub>0</sub>	S <sub>2</sub>	S <sub>2</sub>	S <sub>0</sub>	0	100	00	xx
S <sub>2</sub>	S <sub>0</sub>	S <sub>3</sub>	S <sub>3</sub>	S <sub>0</sub>	0	001	01	xx
S <sub>3</sub>	S <sub>0</sub>	S <sub>4</sub>	S <sub>4</sub>	S <sub>0</sub>	0	001	10	xx
S <sub>4</sub>	S <sub>0</sub>	S <sub>5</sub>	S <sub>5</sub>	S <sub>0</sub>	0	101	00	xx
S <sub>5</sub>	S <sub>0</sub>	S <sub>6</sub>	S <sub>6</sub>	S <sub>0</sub>	0	111	11	01
S <sub>6</sub>	S <sub>0</sub>	S <sub>7</sub>	S <sub>7</sub>	S <sub>0</sub>	0	110	01	10
S <sub>7</sub>	S <sub>0</sub>	S <sub>8</sub>	S <sub>8</sub>	S <sub>0</sub>	0	111	10	11
S <sub>8</sub>	S <sub>0</sub>	S <sub>9</sub>	S <sub>9</sub>	S <sub>0</sub>	0	011	00	xx
S <sub>9</sub>	S <sub>0</sub>	S <sub>10</sub>	S <sub>5</sub>	S <sub>0</sub>	0	101	00	xx
S <sub>10</sub>	S <sub>0</sub>	S <sub>10</sub>	S <sub>10</sub>	S <sub>0</sub>	1	xxx	xx	xx

## Verilog code:

```
1  module FSM(START, ZERO_FLAG, CLK, RST, DONE, opcode, operand1, operand2);
2
3  parameter size = 4;
4
5  input START, ZERO_FLAG, CLK, RST;
6  output reg [size-2:0] opcode;
7  output reg [size-3:0] operand1, operand2;
8  output reg DONE;
9
10 reg [size-1:0] state, nextState;
11 parameter S0=0, S1=1, S2=2, S3=3, S4=4, S5=5, S6=6, S7=7, S8=8, S9=9, S10=10;
12
13 initial begin
14     state <= S0;
15     nextState <= S0;
16 end
17
18 always @(posedge CLK or posedge RST) begin
19
20     if(RST)
21         state <= S0;
22     else
23         state <= nextState;
24 end
25
26 always @(state) begin
27
28     DONE = 0;
29     opcode = 3'b000;
30     operand1 = 2'b00;
31     operand2 = 2'b00;
32
33     case(state)
34     S0: begin
35         opcode = 3'b000;
36     end
37     S1: begin
38         opcode = 3'b100;
39         operand1 = 2'b00;
40     end
41     S2: begin
42         opcode = 3'b001;
43         operand1 = 2'b01;
44     end
45 end
```

```

44     end
45     S3: begin
46         opcode = 3'b001;
47         operand1 = 2'b10;
48     end
49     S4: begin
50         opcode = 3'b101;
51         operand1 = 2'b00;
52     end
53     S5: begin
54         opcode = 3'b111;
55         operand1 = 2'b11;
56         operand2 = 2'b01;
57     end
58     S6: begin
59         opcode = 3'b110;
60         operand1 = 2'b01;
61         operand2 = 2'b10;
62     end
63     S7: begin
64         opcode = 3'b111;
65         operand1 = 2'b10;
66         operand2 = 2'b11;
67     end
68     S8: begin
69         opcode = 3'b011;
70         operand1 = 2'b00;
71     end
72     S9: begin
73         opcode = 3'b101;
74         operand1 = 2'b00;
75     end
76     S10: begin
77         DONE = 1;
78     end
79 endcase
80 end
81
82 always @(state or START or ZERO_FLAG) begin
83
84     nextState = S0;
85

```

```


86     case(state)
87     S0: begin
88         if(START)
89             nextState = S1;
90         end
91     S1: begin
92         nextState = S2;
93     end
94     S2: begin
95         nextState = S3;
96     end
97     S3: begin
98         nextState = S4;
99     end
100    S4: begin
101        if(ZERO_FLAG)
102            nextState = S1;
103        else
104            nextState = S5;
105        end
106    S5: begin
107        nextState = S6;
108    end
109    S6: begin
110        nextState = S7;
111    end
112    S7: begin
113        nextState = S8;
114    end
115    S8: begin
116        nextState = S9;
117    end
118    S9: begin
119        if(ZERO_FLAG)
120            nextState = S10;
121        else
122            nextState = S5;
123        end
124    S10: begin
125        nextState = S10;
126    end
127 endcase
128 end
129 endmodule

```

## ModelSim Testbench:

```
1  module FSM_TB();
2
3      parameter size = 4;
4
5      reg START, ZERO_FLAG, CLK, RST;
6      wire [size-2:0] opcode;
7      wire [size-3:0] operand1, operand2;
8      wire DONE;
9
10     FSM DUT(START, ZERO_FLAG, CLK, RST, DONE, opcode, operand1, operand2);
11
12     always begin
13         CLK = 0; #50;
14         CLK = 1; #50;
15     end
16
17     initial begin
18         START = 0; ZERO_FLAG = 0; RST = 0; #100;
19         START = 1; ZERO_FLAG = 0; RST = 0; #100;
20         START = 0; ZERO_FLAG = 0; RST = 0; #100;
21         START = 0; ZERO_FLAG = 0; RST = 0; #100;
22         START = 0; ZERO_FLAG = 0; RST = 0; #100;
23         START = 0; ZERO_FLAG = 1; RST = 0; #100;
24         START = 0; ZERO_FLAG = 0; RST = 0; #100;
25         START = 0; ZERO_FLAG = 0; RST = 0; #100;
26         START = 0; ZERO_FLAG = 0; RST = 0; #100;
27         START = 0; ZERO_FLAG = 0; RST = 0; #100;
28         START = 0; ZERO_FLAG = 0; RST = 0; #100;
29         START = 0; ZERO_FLAG = 0; RST = 0; #100;
30         START = 0; ZERO_FLAG = 0; RST = 0; #100;
31         START = 0; ZERO_FLAG = 0; RST = 0; #100;
32         START = 0; ZERO_FLAG = 0; RST = 0; #100;
33         START = 0; ZERO_FLAG = 0; RST = 0; #100;
34         START = 0; ZERO_FLAG = 0; RST = 0; #100;
35         START = 0; ZERO_FLAG = 0; RST = 0; #100;
36         START = 0; ZERO_FLAG = 0; RST = 0; #100;
37         START = 0; ZERO_FLAG = 1; RST = 0; #100;
38         START = 0; ZERO_FLAG = 0; RST = 1; #100;
39
40         START = 1; ZERO_FLAG = 0; RST = 0; #100;
41         START = 0; ZERO_FLAG = 0; RST = 0; #100;
42     end
43
44
45 endmodule;
```

## ModelSim Simulation:

 

Comments: By using the flowchart provided in the lab manual, I first drew a state table followed by a state table. Then using the state diagram and table, I used the Moore Model provided in the manual and wrote all the verilog code according to it. For the modelsim testbench I followed the flowchart making sure to making sure to include both decisions yes and no for the decision box “count == 0”. The modesim simulation completely verifies my state diagram and agree with the flowchart as well.



# FSM\_DECO)

## Verilog code:

```
1 module FSM_DECO(opcode, operand1, operand2, alu_opcode, rd_addr1, rd_addr2, wrt_addr, wrt_en, load_data);
2
3 parameter size = 4;
4
5 input [size-2:0] opcode;
6 input [size-3:0] operand1, operand2;
7
8 output reg [size-2:0] alu_opcode;
9 output reg [size-3:0] rd_addr1, rd_addr2, wrt_addr;
10 output reg wrt_en, load_data;
11
12 always @(opcode or operand1 or operand2) begin
13
14     alu_opcode = opcode;
15     wrt_addr = operand1;
16     rd_addr1 = operand1;
17     rd_addr2 = operand2;
18     wrt_en = 1;
19     load_data = 0;
20
21     if(opcode == 3'b000 || opcode == 3'b101)
22         wrt_en = 0;
23     if(opcode == 3'b100)
24         load_data = 1;
25
26 end
27 endmodule
```

## ModelSim Testbench:

```
1 module FSM_DECO_TB();
2
3 parameter size = 4;
4
5 reg [size-2:0] opcode;
6 reg [size-3:0] operand1, operand2;
7
8 wire [size-2:0] alu_opcode;
9 wire [size-3:0] rd_addr1, rd_addr2, wrt_addr;
10 wire wrt_en, load_data;
11
12 FSM_DECO DUT(opcode, operand1, operand2, alu_opcode, rd_addr1, rd_addr2, wrt_addr, wrt_en, load_data);
13
14 initial begin
15     opcode = 3'b000; operand1 = 2'b00; operand2 = 2'b01; #100;
16     opcode = 3'b001; operand1 = 2'b00; operand2 = 2'b01; #100;
17     opcode = 3'b010; operand1 = 2'b00; operand2 = 2'b01; #100;
18     opcode = 3'b011; operand1 = 2'b00; operand2 = 2'b01; #100;
19     opcode = 3'b100; operand1 = 2'b00; operand2 = 2'b01; #100;
20     opcode = 3'b101; operand1 = 2'b00; operand2 = 2'b01; #100;
21     opcode = 3'b110; operand1 = 2'b00; operand2 = 2'b01; #100;
22     opcode = 3'b111; operand1 = 2'b00; operand2 = 2'b01; #100;
23
24 end
25 endmodule
```



# FIBO\_FSM)


## Verilog code:

```
1 module FIBO_FSM(START, CLK, RST, ZERO_FLAG, wrt_addr, wrt_en, clk, load_data, rd_addr1, rd_addr2, alu_opcode, DONE);
2
3 parameter size = 4;
4
5 input START, ZERO_FLAG, CLK, RST;
6
7 output [size-2:0] alu_opcode;
8 output [size-3:0] rd_addr1, rd_addr2, wrt_addr;
9 output clk, wrt_en, load_data, DONE;
10
11 wire [size-2:0] opcode;
12 wire [size-3:0] operand1, operand2;
13
14 FSM_F1(START, ZERO_FLAG, CLK, RST, DONE, opcode, operand1, operand2);
15 FSM_DECO_F2(opcode, operand1, operand2, alu_opcode, rd_addr1, rd_addr2, wrt_addr, wrt_en, load_data);
16
17 assign clk = CLK;
18
19 endmodule
20
```

## ModelSim Testbench:

```
1 module FIBO_FSM_TB();
2
3 parameter size = 4;
4
5 reg START, ZERO_FLAG, CLK, RST;
6 wire [size-2:0] alu_opcode;
7 wire [size-3:0] rd_addr1, rd_addr2, wrt_addr;
8 wire clk, wrt_en, load_data, DONE;
9
10 FIBO_FSM DUT(START, CLK, RST, ZERO_FLAG, wrt_addr, wrt_en, clk, load_data, rd_addr1, rd_addr2, alu_opcode, DONE);
11
12
13 always begin
14     CLK = 0; #50;
15     CLK = 1; #50;
16 end
17
18 initial begin
19     START = 0; ZERO_FLAG = 0; RST = 0; #100;
20     START = 1; ZERO_FLAG = 0; RST = 0; #100;
21     START = 0; ZERO_FLAG = 0; RST = 0; #100;
22     START = 0; ZERO_FLAG = 0; RST = 0; #100;
23     START = 0; ZERO_FLAG = 0; RST = 0; #100;
24     START = 0; ZERO_FLAG = 1; RST = 0; #100;
25     START = 0; ZERO_FLAG = 0; RST = 0; #100;
26     START = 0; ZERO_FLAG = 0; RST = 0; #100;
27     START = 0; ZERO_FLAG = 0; RST = 0; #100;
28     START = 0; ZERO_FLAG = 0; RST = 0; #100;
29     START = 0; ZERO_FLAG = 0; RST = 0; #100;
30     START = 0; ZERO_FLAG = 0; RST = 0; #100;
31     START = 0; ZERO_FLAG = 0; RST = 0; #100;
32     START = 0; ZERO_FLAG = 0; RST = 0; #100;
33     START = 0; ZERO_FLAG = 0; RST = 0; #100;
34     START = 0; ZERO_FLAG = 0; RST = 0; #100;
35     START = 0; ZERO_FLAG = 0; RST = 0; #100;
36     START = 0; ZERO_FLAG = 0; RST = 0; #100;
37     START = 0; ZERO_FLAG = 0; RST = 0; #100;
38     START = 0; ZERO_FLAG = 1; RST = 0; #100;
39     START = 0; ZERO_FLAG = 0; RST = 1; #100;
40
41     START = 1; ZERO_FLAG = 0; RST = 0; #100;
42     START = 0; ZERO_FLAG = 0; RST = 0; #100;
43 end
44 endmodule
45
```

## ModelSim Simulation:

 

Comments: FIBO\_FSM is the combination of FSM and FSM\_DECO. It is written using top level design and the modelsim simulations verifies that the outputs are correct.


# FIBO\_CALCULATOR)

## Verilog code:

```
1 module FIBO_CALCULATOR(START, CLK, RST, COUNT, DONE, DATA);
2
3 parameter size = 4;
4
5 input [size-1:0] COUNT;
6 input START, CLK, RST;
7
8 output [size-1:0] DATA;
9 output DONE;
10
11 wire [size-2:0] alu_opcode;
12 wire [size-3:0] rd_addr1, rd_addr2, wrt_addr;
13 wire clk, wrt_en, load_data;
14 wire zero_flag;
15
16 FIBO_FSM F1(START, CLK, RST, zero_flag, wrt_addr, wrt_en, clk, load_data, rd_addr1, rd_addr2, alu_opcode, DONE);
17 FIBO_DATAPATH D1(wrt_addr, wrt_en, clk, load_data, rd_addr1, rd_addr2, alu_opcode, COUNT, zero_flag, DATA);
18
19 endmodule
20
```
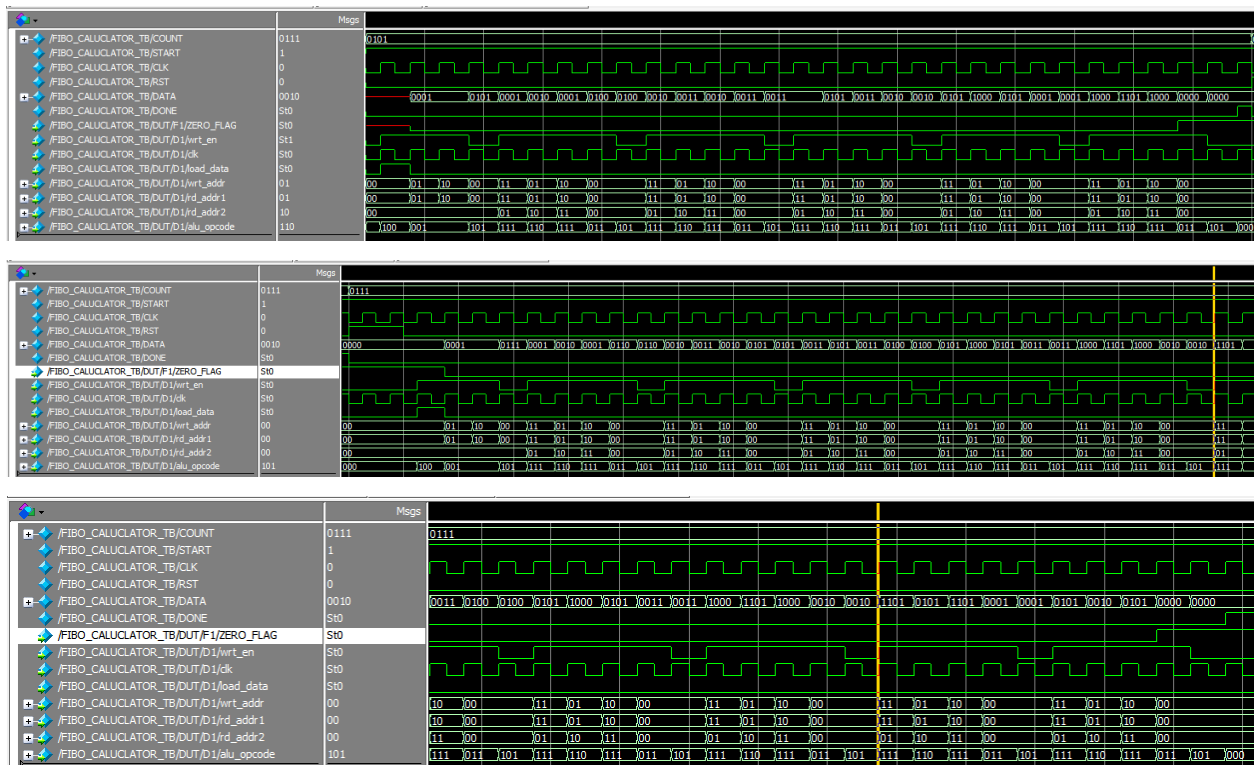
## ModelSim Testbench:

```
1 module FIBO_CALCULATOR_TB();
2 parameter size = 4;
3
4 reg [size-1:0] COUNT;
5 reg START, CLK, RST;
6
7 wire [size-1:0] DATA;
8 wire DONE;
9
10 FIBO_CALCULATOR DUT(START, CLK, RST, COUNT, DONE, DATA);
11
12 always begin
13     CLK = 0; #50;
14     CLK = 1; #50;
15 end
16
17 initial begin
18     START = 1; RST = 0; COUNT = 4'b0101; #3000;
19     START = 1; RST = 1; COUNT = 4'b0111; #200;
20     START = 1; RST = 0; COUNT = 4'b0111; #100;
21 end
22
23 endmodule
```



Comments: This is the top level design for the whole implementation of fibonacci calculator. This includes the FIBO\_FSM and the DATAPATH. The FIBO\_FSM controls the outputs and uses the datapath to find the fibonacci. The modelsim simulation is used to first find the fibonacci for 5 sequence then after a reset it calculates for 7 sequences. The simulation shows that the output is correct for the 5 sequences but for 7 sequences since the number gets larger than what 4 bit can store, the output is not as expected. Since we have used a parameterized approach we can easily increase the bit size and overcome this issue. Overall the simulation is successful in showing a correct fibonacci sequence.

## FMAX)

Slow 1200mV 85C Model Fmax Summary				
	Fmax	Restricted Fmax	Clock Name	Note
1	401.12 MHz	250.0 MHz	CLK	limit due to minimum period restriction (max I/O toggle rate)
2	531.35 MHz	257.2 MHz	FIBO_FSM:F1 FSM:F1 state.S0	limit due to hold check

Comments: Overall, the fibonacci fsm calculator is written in a scalable way to ensure that number of bits can be increased, furthermore every verilog code written is tested using the modelsim testbench to look for any anomaly. I can safely say that my modelsim simulations act accordingly and that the requirements of the lab have been met.